

Series and Parallel Resistors

First, let's have a summary of the types of quantities so far introduced, and then we will derive two new results.

| Quantity | Usual Variable Name | Standard Unit | Unit Abbreviation |
|----------------------|---------------------|---------------|-------------------|
| Charge | Q | Coulomb | C |
| Current | I | Ampere | A |
| Energy | E | Joule | J |
| Power | P | Watt | W |
| Electrical Potential | V | Volt | V |
| Resistance | R | Ohm | Ω |

Charge, like mass, cannot be created or destroyed. Because like charges repel, charge never piles up. In other words, all ^{almost} circuit elements are neutral, even batteries.


Resistors have a linear I - V curve. The resistance of a resistor, R , is the slope of the line, so

$$V = IR$$

Before leaving the summary, let's also get all the jargon on the table:

| <u>Term</u> | <u>Synonyms or Jargon</u> |
|----------------------|---|
| Current | Sometimes called "amperage" |
| Electrical Potential | { Usually just "potential" Very often called "voltage" |
| Power | often called "wattage" |
| Ampere | often shortened to "Amp" |

Fundamental Formulas

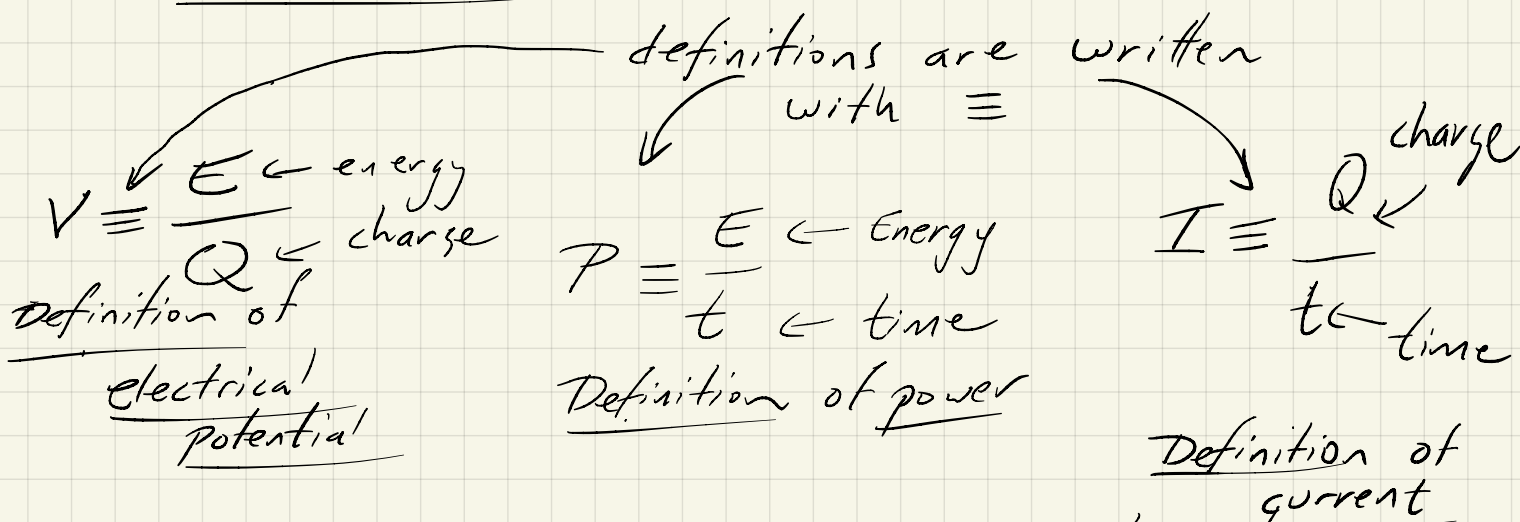


The formula $V = IR$ is extremely important, but it is a property of an ideal resistor. Real resistors are so close to ideal, this formula is known as "ohm's Law."


That's the summary. Onward to two new results....

1. Resistors in Series

Consider this circuit:

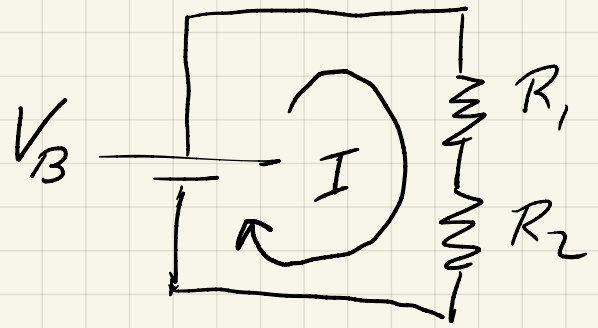


Or equivalently:

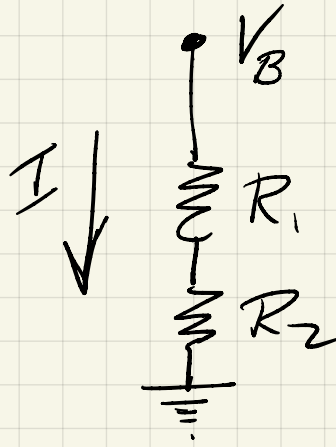

If V_B (the voltage of the battery) and R_1 and R_2 are known, what is I ?

The trick is to label one more unknown:

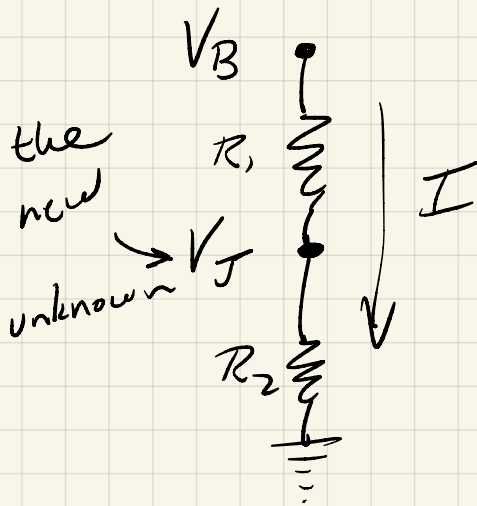

V_J is the voltage on the wire connecting the two resistors. The voltage drop across R_1 is

$V_B - V_J$ and this must be IR_1 by Ohm's Law

The voltage drop across R_2 is $V_J - 0 = V_J$ and this must be IR_2 (again by Ohm's Law)


$$\left. \begin{array}{l} V_B - V_J = IR_1 \\ V_J = IR_2 \end{array} \right\} \text{ADD THESE EQUATIONS TO GET}$$

$$V_B - \cancel{V_J} + \cancel{V_J} = IR_1 + IR_2$$


$$V_B = I(R_1 + R_2) \leftarrow \begin{array}{l} \text{Resistors in series add} \\ V = IR_{\text{Series}} \quad R_{\text{Series}} = R_1 + R_2 \end{array}$$

2. Resistors in Parallel

Consider this circuit:

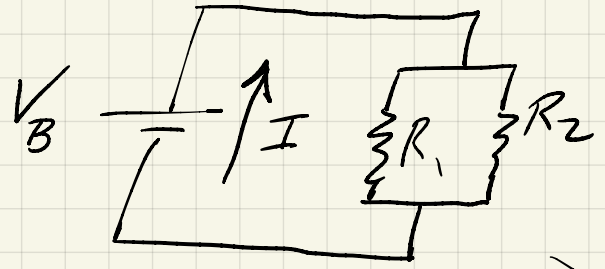


Or equivalently:

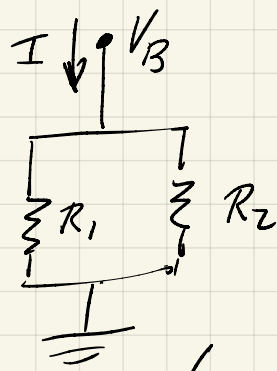

If V_B , R_1 , and R_2 are known, what is I ?

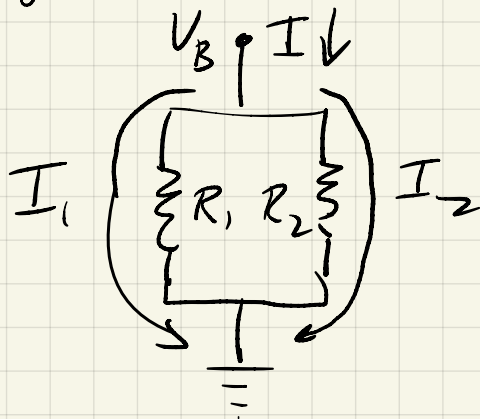Again the trick is to label some unknowns:



I_1 is the current flowing through R_1 ,

I_2 is the current flowing through R_2

The total current going from the battery to ground divides up and goes through the two resistors:

$$I = I_1 + I_2$$

By Ohm's Law for R_1 : $V_B = I_1 R_1$ or $I_1 = \frac{V_B}{R_1}$

By Ohm's Law for R_2 : $V_B = I_2 R_2$ or $I_2 = \frac{V_B}{R_2}$

$$\text{So } I = \frac{V_B}{R_1} + \frac{V_B}{R_2} = V_B \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

Or $V_B = I R_{\text{Parallel}}$ where

$$R_{\text{Parallel}} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$

for resistors in parallel

The weird result